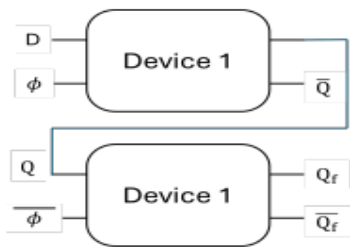


Q1.


### Scenario 1:

A classroom has **three** temperature sensors to control the temperature of the room by controlling the air conditioner installed in that room. The temperature sensors produce a high output if the temperature crosses a certain threshold. The air conditioner turns **on** if the outputs of all three sensors are **high**, otherwise it remains **off**.

### Scenario 2:



**Figure: 1**

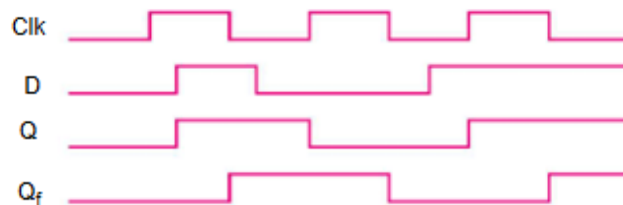

**Figure: 2**

**Figure 2** shows the output waveshape of the device implemented in **Figure 1**.

(a)	<b>Identify</b> the logic circuit required to implement the system mentioned in scenario 1 and implement the circuit using <b>2:1 mux</b> .	[5]
(b)	<b>Identify</b> the circuit implemented in <b>Figure 1</b> from the timing diagram of <b>Figure 2</b> . Also identify <b>Device 1</b> shown in <b>Figure 1</b> .	[3]
(c)	<b>Draw</b> the circuit of <b>Device 1</b> using transmission gates.	[3]
(d)	<b>Explain</b> why <b>n-MOS</b> pass transistors produce good 0 and bad 1, and <b>p-MOS</b> pass transistors produce bad 0 and good 1 with proper mathematical justification.	[4]