

CSE 460: VLSI Design

Lecture 9: Finite State Machines (part 2)

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)


Clock cycle:	t_0	t_1	t_2	t_3	t_4	t_5	t_6	t_7	t_8	t_9	t_{10}
w :	0	1	0	1	1	0	1	1	1	0	1
z :	0	0	0	0	1	0	0	1	1	0	0

Figure 6.22 Sequences of input and output signals.

Steps->

- State diagram
- State table
- State assigned table
- K-map
- Circuit

 Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)



Steps->

- State diagram
- State table
- State assigned table
- K-map
- Circuit

Figure 6.23 State diagram of an FSM that realizes the task in Figure 6.22.

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)

Present state	Next state		Output z	
	$w = 0$	$w = 1$	$w = 0$	$w = 1$
A	A	B	0	0
B	A	B	0	1

Figure 6.24 State table for the FSM in Figure 6.23.

Steps->

- State diagram
- **State table**
- **State assigned table**
- K-map
- Circuit

	Present state	Next state		Output	
		$w = 0$	$w = 1$	$w = 0$	$w = 1$
	y	Y	Y	z	z
A	0	0	1	0	0
B	1	0	1	0	1

Figure 6.25 State-assigned table for the FSM in Figure 6.24.

Note that,

- $Y = f(w, y)$
- $z = f(w, y)$

Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)

Y =>

y \ w	0	1
0	0	1
1	0	1

$$Y = w$$

Z =>

y \ w	0	1
0	0	0
1	0	1

$$z = wy$$


Steps->

- State diagram
- State table
- State assigned table
- **K-map** (Y and z)
- Circuit

Note that,

- $Y = f(w, y)$
- $z = f(w, y)$

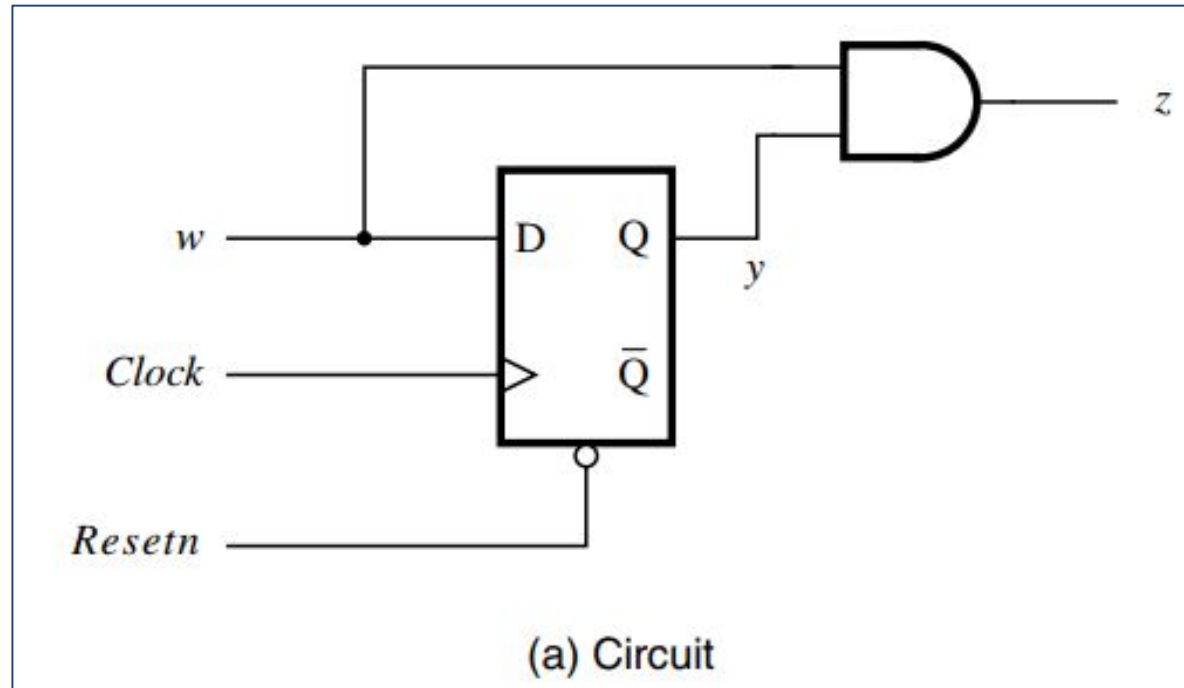Example 2: A Simple Input Pattern ('11' Overlapping Sequence) Detection Circuit (Mealy Type)



Steps->

- State diagram
- State table
- State assigned table
- K-map
- **Circuit**

Encoding Schemes (State Assignment)

Consider a state assigned table below:

	Present state $y_2 y_1$	Next state		Output z
		$w=0$	$w=1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	10	0
C	10	00	10	1
	11	dd	dd	d

Schemes->

- **Binary encoding**
- Gray encoding
- One-hot encoding

Encoding Schemes (State Assignment)

Consider another state assigned table below:

	Present state $y_2 y_1$	Next state		Output z
		$w=0$	$w=1$	
		$Y_2 Y_1$	$Y_2 Y_1$	
A	00	00	01	0
B	01	00	11	0
C	11	00	11	1
	10	dd	dd	d

Schemes->

- Binary encoding
- **Gray encoding**
- One-hot encoding

Decimal Number

4 bit Binary
Number

4 bit Gray
Code

ABCD

G₁G₂G₃G₄

0
1
2
3
4
5
6
7
8
9
10
11
12
13
14
15

0 0 0 0
0 0 0 1
0 0 1 0
0 0 1 1
0 1 0 0
0 1 0 1
0 1 1 0
0 1 1 1
1 0 0 0
1 0 0 1
1 0 1 0
1 0 1 1
1 1 0 0
1 1 0 1
1 1 1 0
1 1 1 1

0 0 0 0
0 0 0 1
0 0 1 1
0 0 1 0
0 1 1 0
0 1 1 1
0 1 0 1
0 1 0 0
1 1 0 0
1 1 0 1
1 1 1 1
1 1 1 0
1 0 1 0
1 0 1 1
1 0 0 1
1 0 0 0

Encoding Schemes (State Assignment)

Consider another state assigned table below:

	Present state $y_3y_2y_1$	Next state		Output z
		$w = 0$	$w = 1$	
		$Y_3Y_2Y_1$	$Y_3Y_2Y_1$	
A	0 0 1	0 0 1	0 1 0	0
B	0 1 0	0 0 1	1 0 0	0
C	1 0 0	0 0 1	1 0 0	1

Schemes->

- Binary encoding
- Gray encoding
- **One-hot encoding**

How many flipflops are required? **Ans: 3**