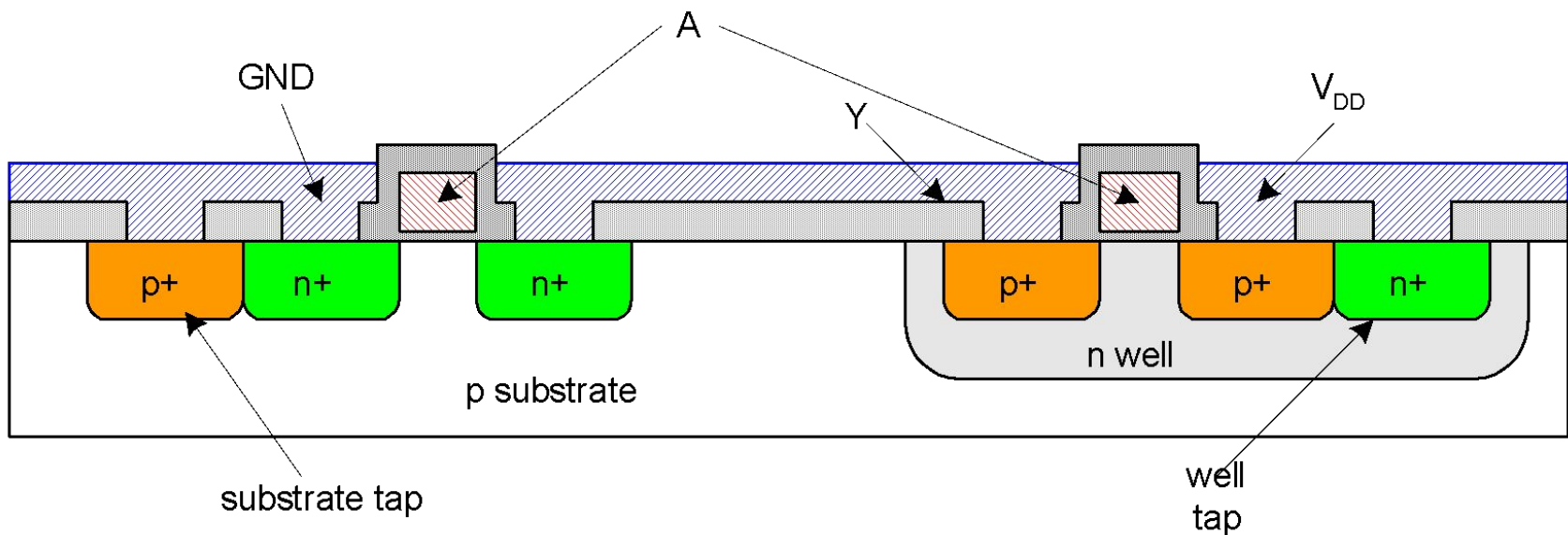


Lecture 12: Layout & Stick Diagrams


Inverter Cross-section

- ❑ Substrate must be tied to GND and n-well to V_{DD}
- ❑ Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- ❑ Use heavily doped well and substrate contacts / taps




Inverter Top View

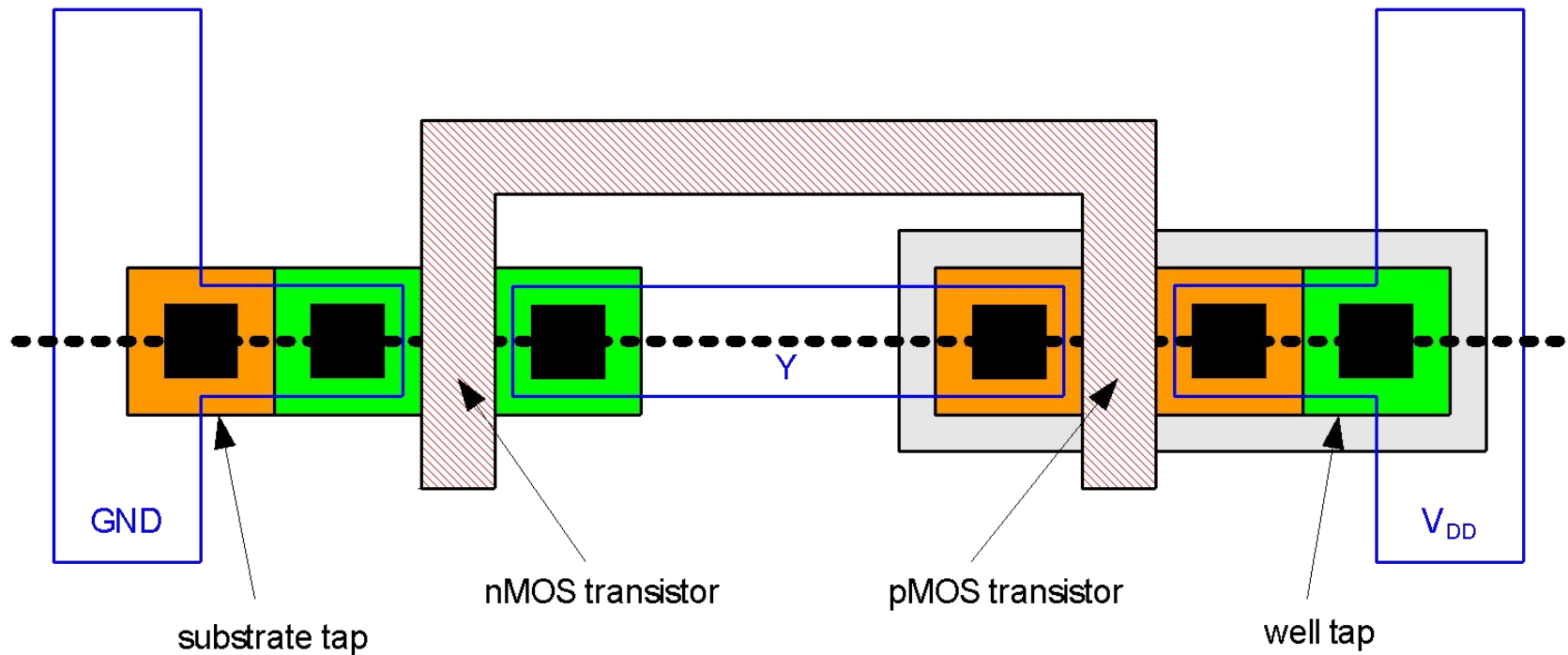
- ❑ Transistors and wires are defined by *masks*
- ❑ Cross-section taken along dashed line



Standard Cell Layout

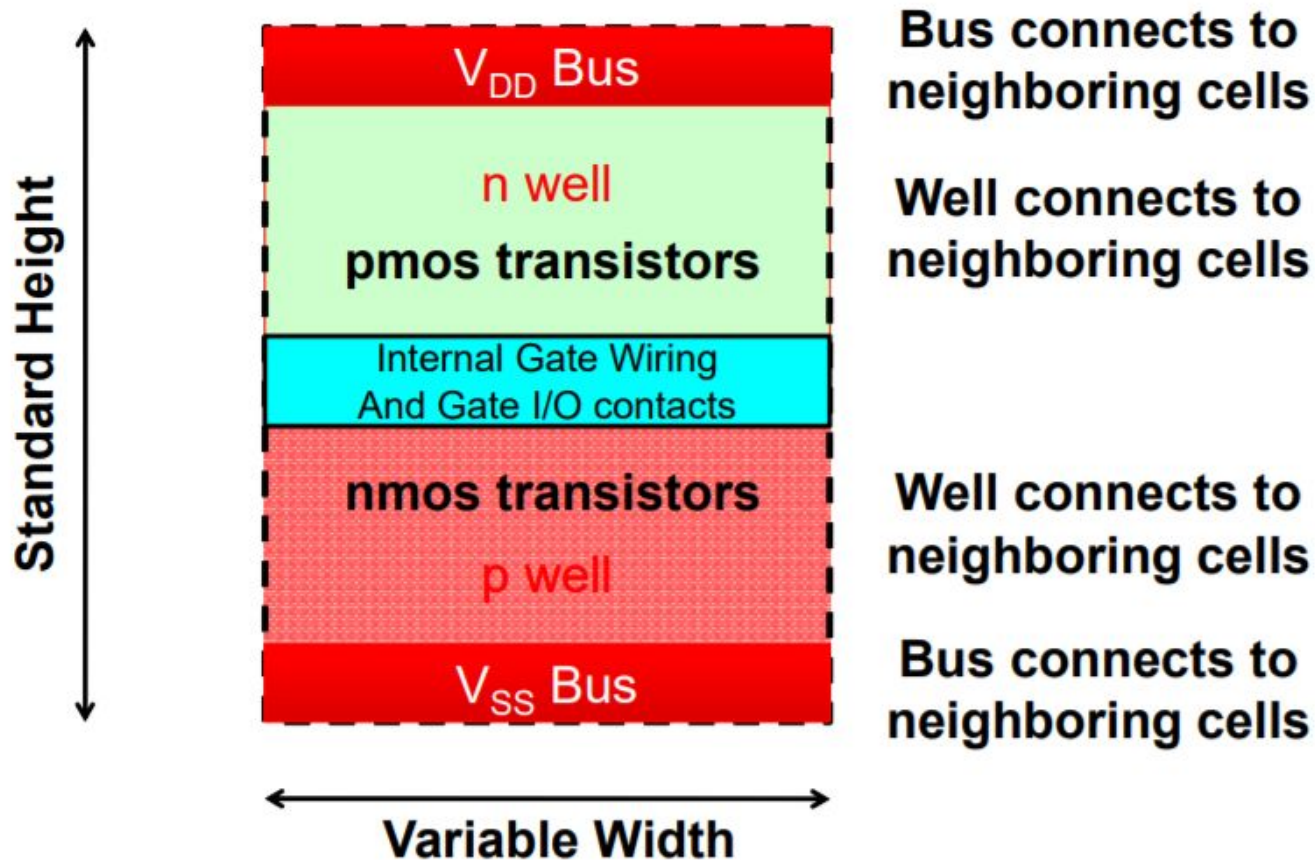

Example: Inverter

 

Gate Layout


- ❑ Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
- ❑ Standard cell design methodology
 - V_{DD} and GND should be about standard height
 - Adjacent gates should satisfy design rules
 - nMOS at bottom and pMOS at top
 - All gates include well and substrate contacts

Layout

- ❑ Chips are specified with set of masks
- ❑ Minimum dimensions of masks determine transistor size (and hence speed, cost, and power)
- ❑ Feature size f = distance between source and drain
 - Set by minimum width of polysilicon
- ❑ Feature size improves 30% every 3 years or so
- ❑ Normalize for feature size when describing design rules
- ❑ Express rules in terms of $\lambda = f/2$
 - E.g. $\lambda = 0.3 \mu\text{m}$ in $0.6 \mu\text{m}$ process

Simplified Design Rules

 
- ❑ Conservative rules to get you started



Source and Drain


- ❑ We will follow the convention: current always flows from top to bottom in an electronic circuit
 - For pMOS transistor:
 - Carrier: holes (+)
 - Top node: Source
 - Bottom node: Drain
 - For nMOS transistor:
 - Carrier: electrons (-)
 - Top node: Drain
 - Bottom node: Source

Example: Inverter


 


3-input NAND Gate

 - ❑ Y pulls low if ALL inputs are 1
- ❑ Y pulls high if ANY input is 0




Example: NAND3

  


 Example: NAND3

- ❑ Horizontal N-diffusion and p-diffusion strips
- ❑ Vertical polysilicon gates
- ❑ Metal1 V_{DD} rail at top
- ❑ Metal1 GND rail at bottom
- ❑ 32λ by 40λ





Example: NAND3

 


Wiring Tracks

  - ❑ A *wiring track* is the space required for a wire
 - 4λ width, 4λ spacing from neighbor = 8λ pitch
- ❑ Transistors also consume one wiring track




Well spacing

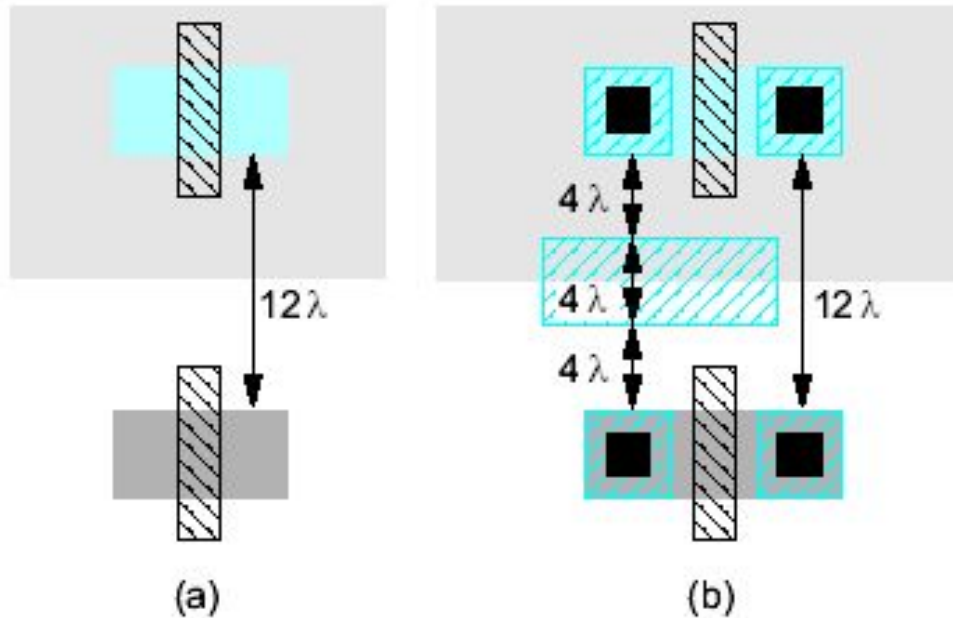- ❑ Wells must surround transistors by 6λ
 - Implies 12λ between opposite transistor flavors
 - Leaves room for one wire track



Stick Diagrams

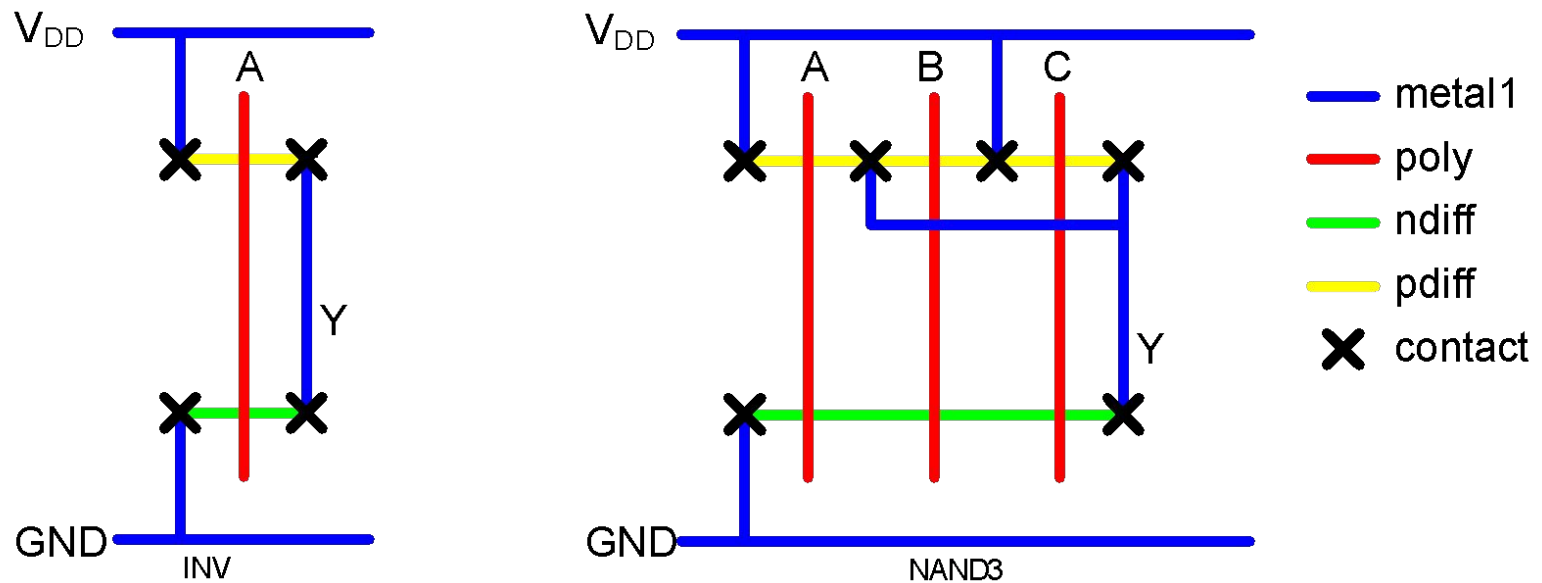
- *Stick diagrams* help plan layout quickly
 - Need not be to scale
 - Draw with color pencils or dry-erase markers



Area Estimation

- Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ

 
Parallel tracks along the width = 4 metals





Area Estimation

- Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ

 Parallel tracks along the height = 3 metals + 2 diff




$$Y = \overline{AB} \text{ (2 NAND)}$$

  


$$Y = \overline{AB} \quad (2 \text{ NAND})$$

 Parallel tracks along the width = 3 metals
width = $3 \times 8\lambda = 24\lambda$





$$Y = \overline{AB} \quad (2 \text{ NAND})$$

 Parallel tracks along the height = 3 metals + 2 diff
height = $5 \times 8\lambda = 40\lambda$



  
$$Y = \overline{ABC} \quad (3 \text{ NAND})$$



$$Y = \overline{ABC} \quad (3 \text{ NAND})$$


Parallel tracks along the width = 4 metals
 
$$\text{width} = 4 \times 8\lambda = 32\lambda$$





$$Y = \overline{ABC} \quad (3 \text{ NAND})$$

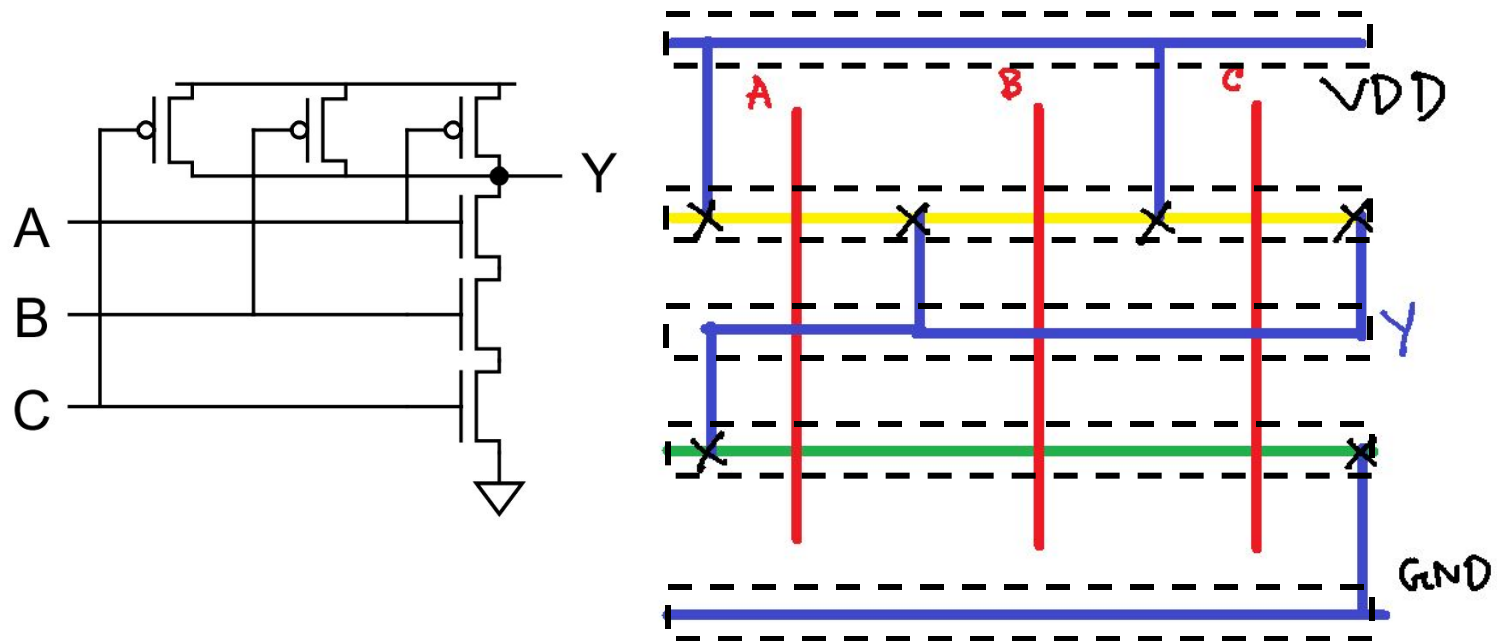Parallel tracks along the height = 3 metals + 2 diff
height = $5 \times 8\lambda = 40\lambda$




  
$$Y = \overline{A + B} \quad (2 \text{ NOR})$$





$$Y = \overline{A + B} \text{ (2 NOR)}$$

  Parallel tracks along the width = 3 metals
width = $3 \times 8\lambda = 24\lambda$





$$Y = \overline{A + B} \text{ (2 NOR)}$$

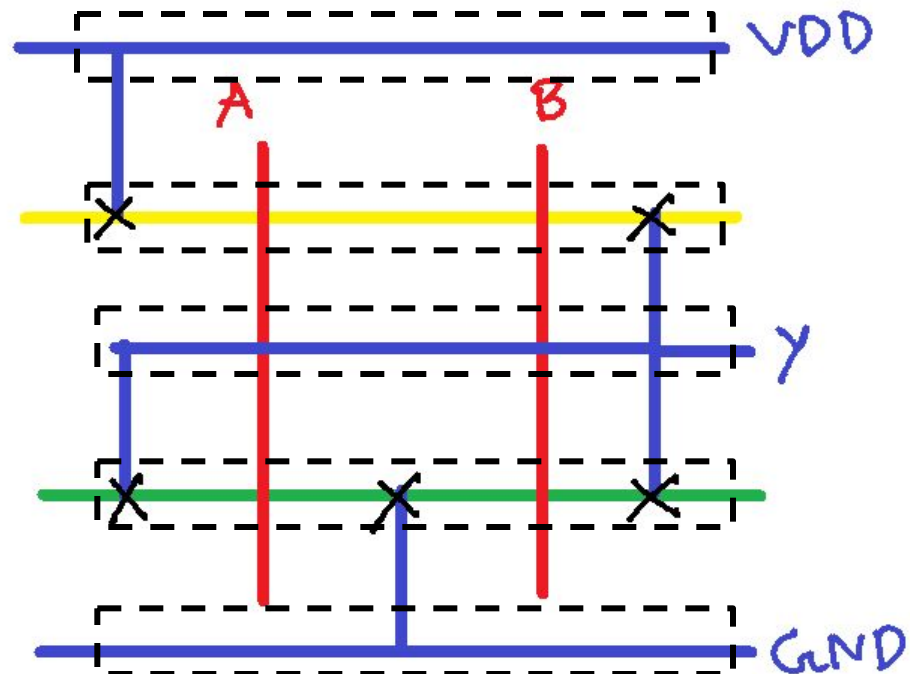 Parallel tracks along the height = 3 metals + 2 diff
width = $5 \times 8\lambda = 40\lambda$



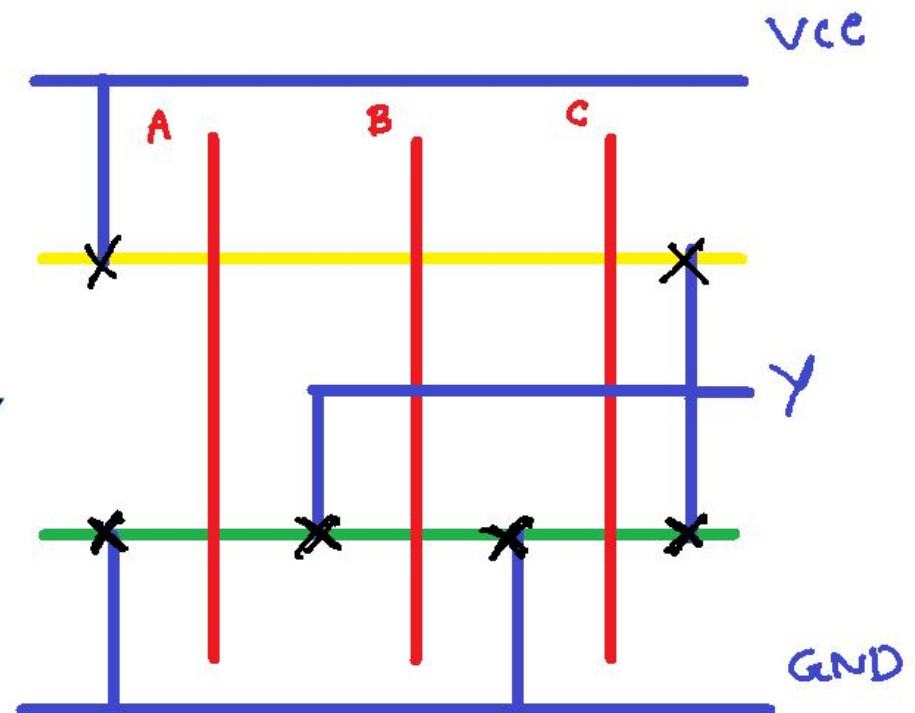 
$$Y = \overline{A + B + C} \quad (3 \text{ NOR})$$




$$Y = \overline{A + B + C} \text{ (3 NOR)}$$

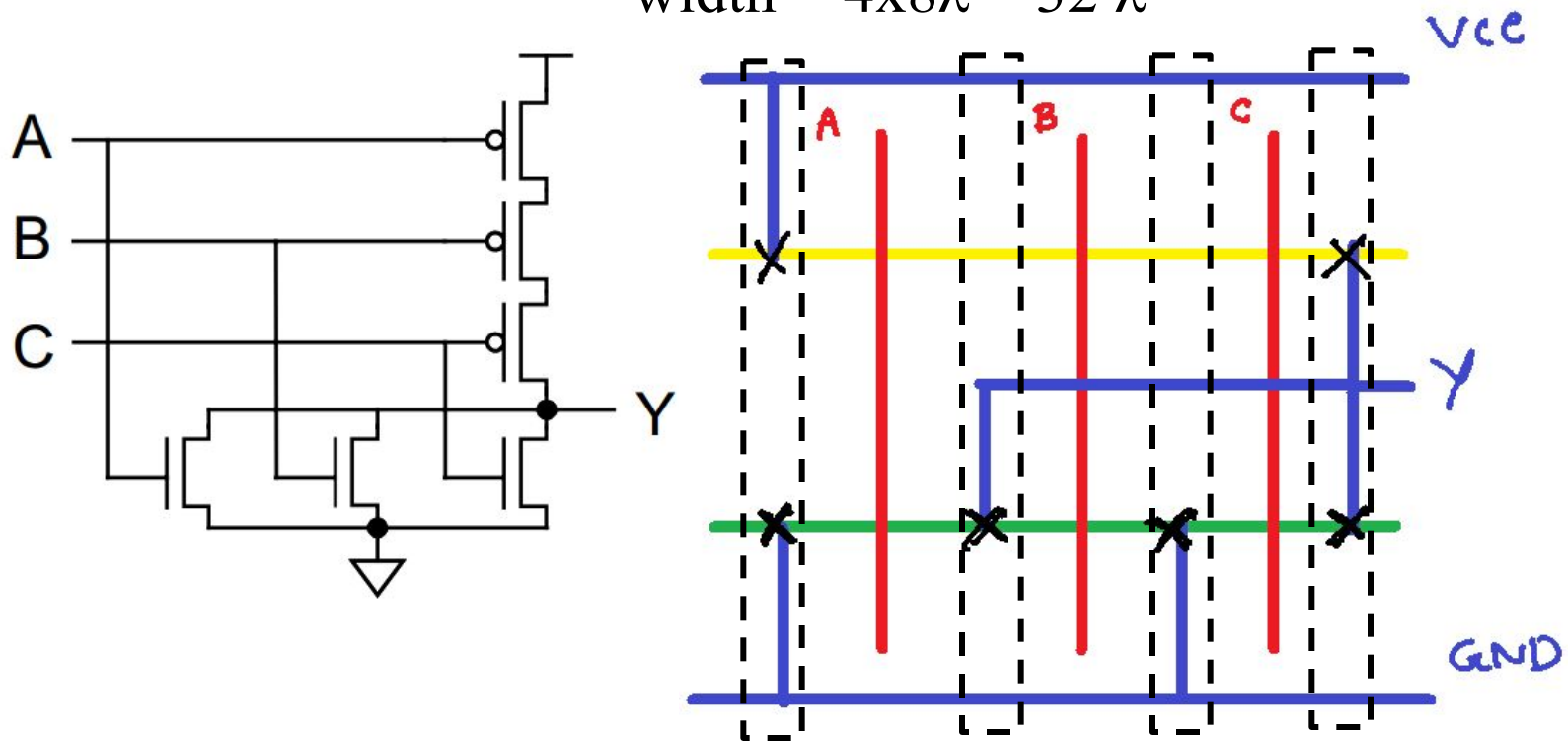Parallel tracks along the width = 4 metals
width = $4 \times 8\lambda = 32\lambda$





$$Y = \overline{A + B + C} \text{ (3 NOR)}$$

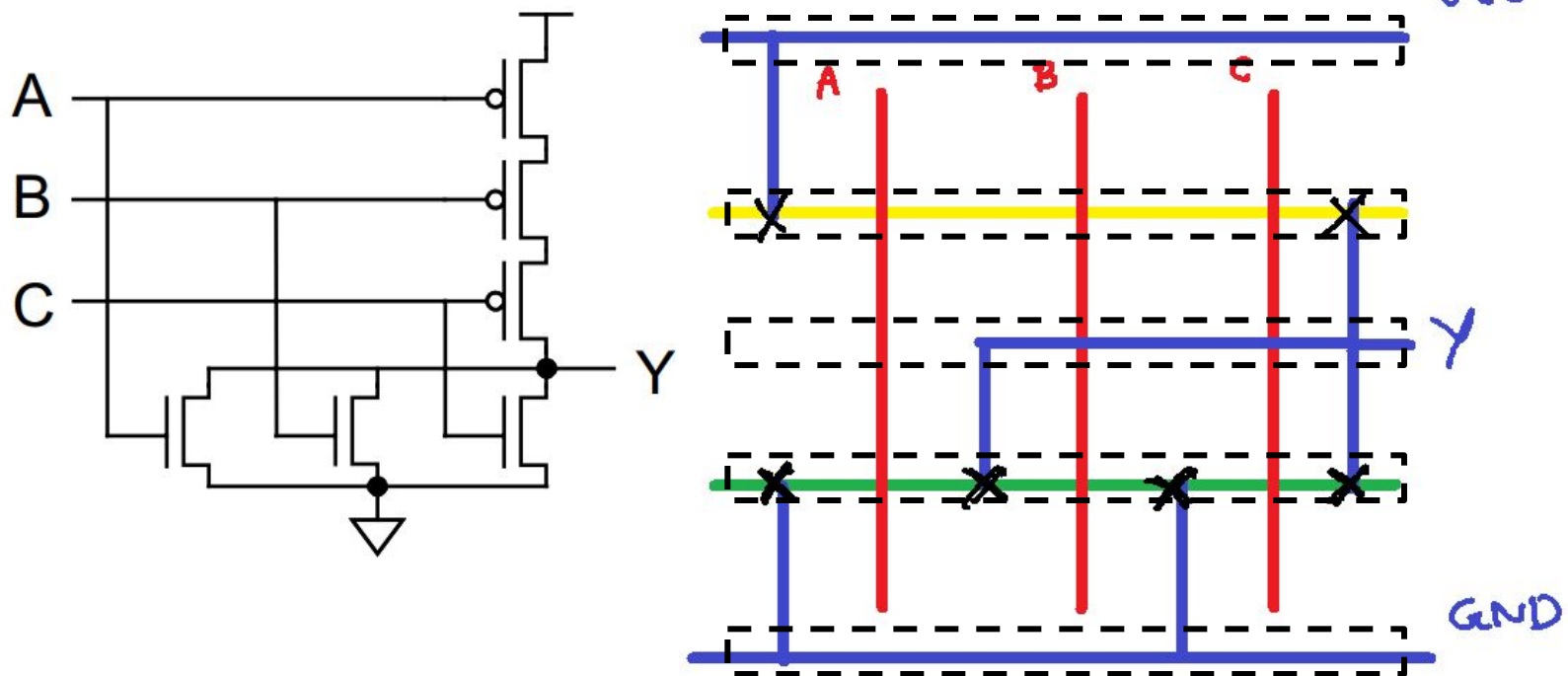Parallel tracks along the height = 3 metals + 2 diff
height = $5 \times 8\lambda = 40\lambda$




  
$$Y = \overline{A + B + C + D} \quad (4 \text{ NOR})$$





$$Y = \overline{A + B + C + D} \quad (4 \text{ NOR})$$

  Parallel tracks along the width = 5 metals
width = $5 \times 8\lambda = 40\lambda$





$$Y = \overline{A + B + C + D} \quad (4 \text{ NOR})$$

  Parallel tracks along the height = 3 metals + 2 diff
height = $5 \times 8\lambda = 40\lambda$




$$Y = \overline{AB + CD}$$

  

$$Y = \overline{AB + CD}$$



Parallel tracks along the width = 5 metals

width = $5 \times 8\lambda = 40\lambda$

 


$$Y = \overline{AB + CD}$$

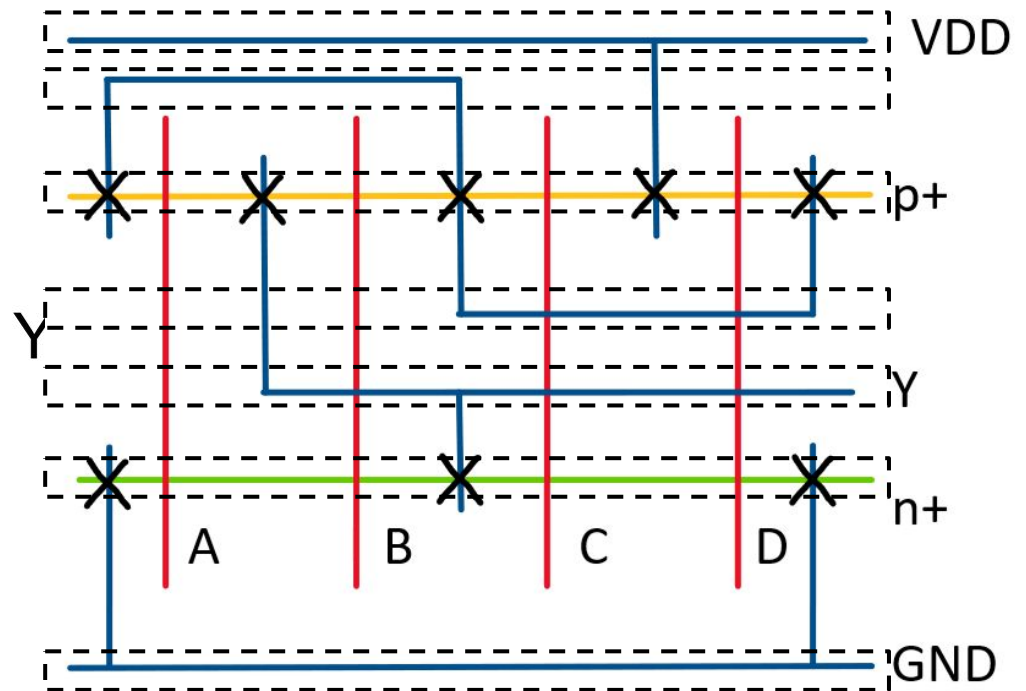 
Parallel tracks along the height = 5 metals + 2 diff
width = $7 \times 8\lambda = 56\lambda$



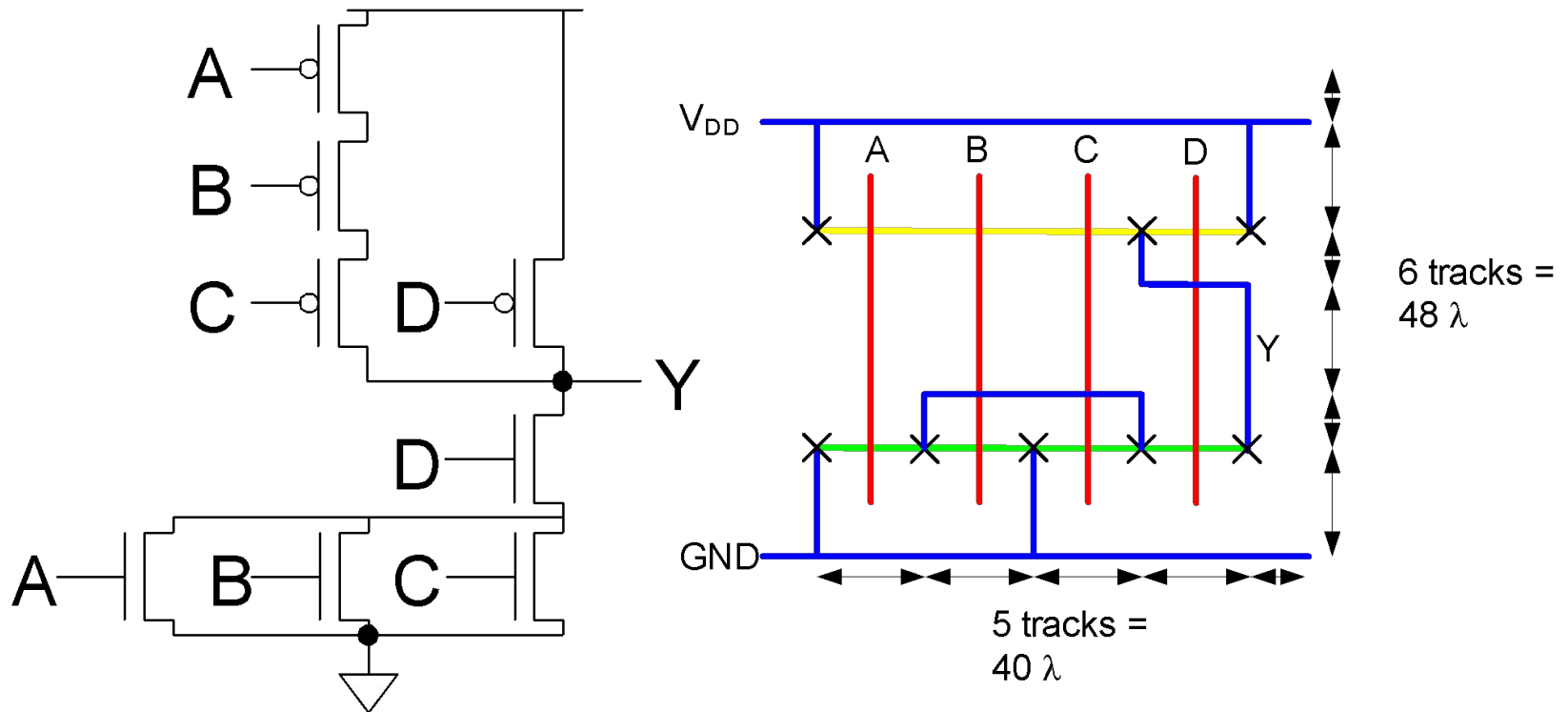
$$Y = \overline{(A + B + C)D} \text{ (03AI)}$$



Stick Diagram Optimization

 


3-NAND

 


After Optimization

Stick Diagram Optimization

 



3-NOR

 

After Optimization



Alternate Representations $A(B + C)$

$$\overline{A(B + C)}$$

  



Alternate Representations

$$\overline{A(B + C)}$$

  

Alternate Representations

$$\overline{AB + C}$$

  

Alternate Representations

$$\overline{AB + C}$$

