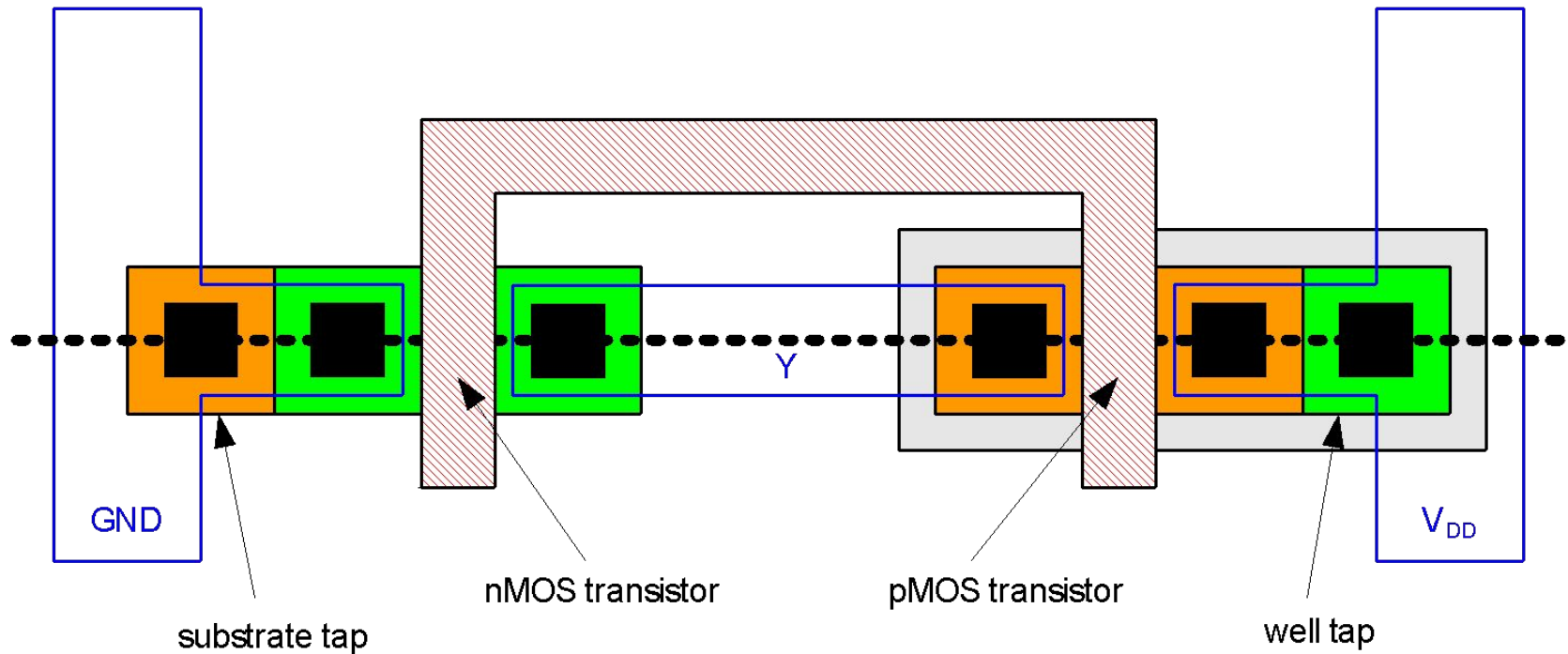


Lecture 10: Layout & Stick Diagrams


Inverter Top View

- ❑ Transistors and wires are defined by *masks*
- ❑ Cross-section taken along dashed line



Inverter Cross-section

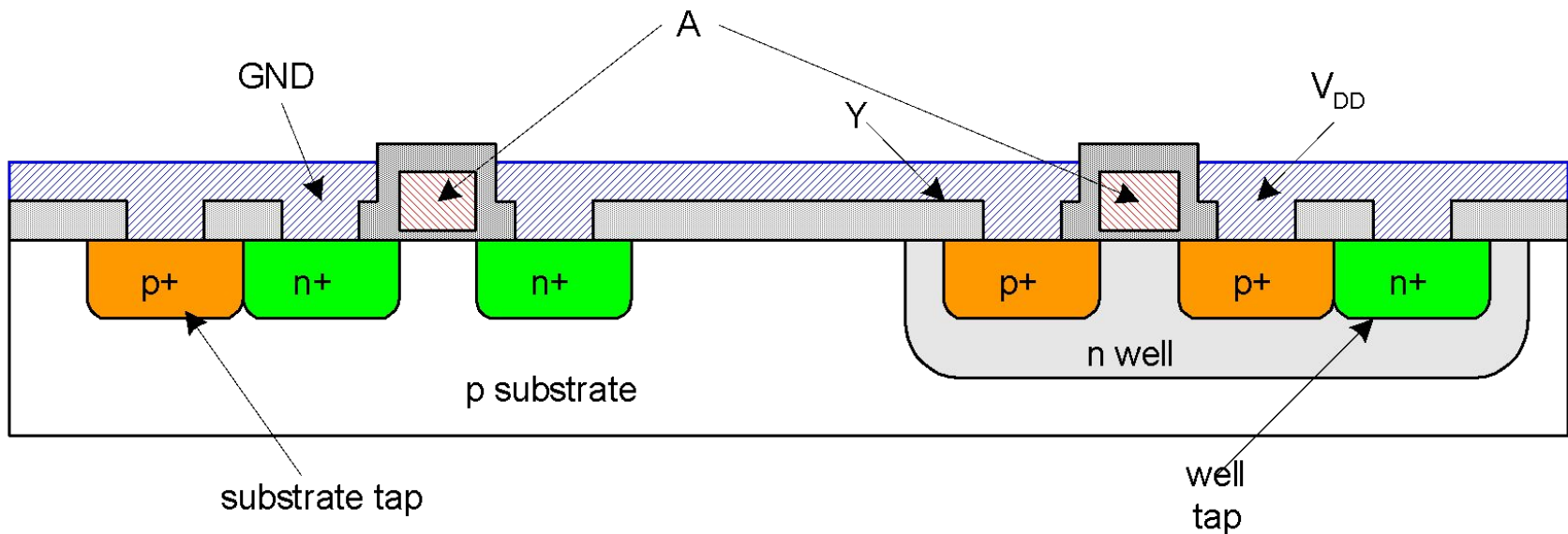
- ❑ Substrate must be tied to GND and n-well to V_{DD}
- ❑ Metal to lightly-doped semiconductor forms poor connection called Shottky Diode
- ❑ Use heavily doped well and substrate contacts / taps



Gate Layout


- ❑ Layout can be very time consuming
 - Design gates to fit together nicely
 - Build a library of standard cells
- ❑ Standard cell design methodology
 - V_{DD} and GND should abut (standard height)
 - Adjacent gates should satisfy design rules
 - nMOS at bottom and pMOS at top
 - All gates include well and substrate contacts

Standard Cell Layout

 

Simplified Design Rules

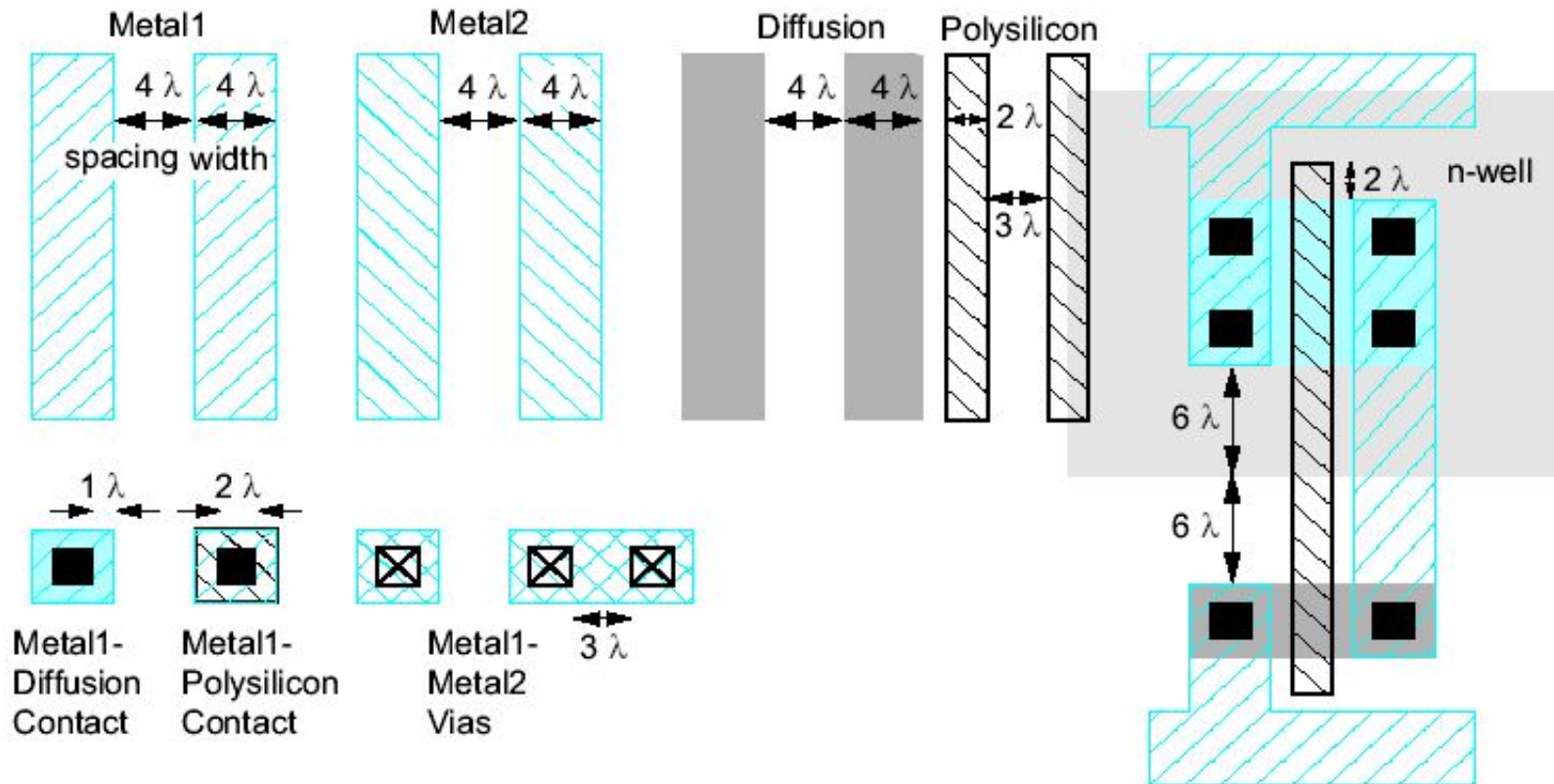
- ❑ Conservative rules to get you started



Source and Drain

- ❑ We will follow the convention: current always flows from top to bottom in an electronic circuit
 - For pMOS transistor:
 - Carrier: holes (+)
 - Top node: Source
 - Bottom node: Drain
 - For nMOS transistor:
 - Carrier: electrons (-)
 - Top node: Drain
 - Bottom node: Source

Example: Inverter

 


3-input NAND Gate


- ☐ Y pulls low if ALL inputs are 1
- ☐ Y pulls high if ANY input is 0

 Example: NAND3

- ❑ Horizontal N-diffusion and p-diffusion strips
- ❑ Vertical polysilicon gates
- ❑ Metal1 V_{DD} rail at top
- ❑ Metal1 GND rail at bottom
- ❑ 32λ by 40λ




Example: NAND3

 



Stick Diagrams

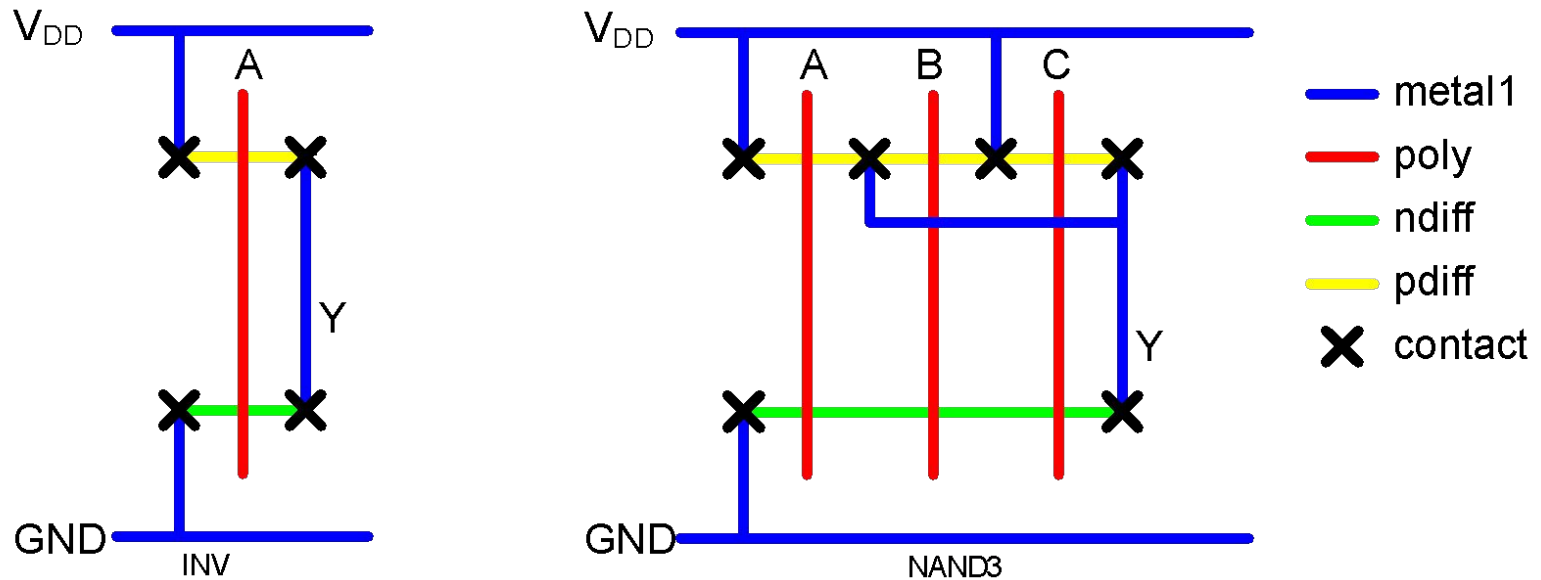- *Stick diagrams* help plan layout quickly
 - Need not be to scale
 - Draw with color pencils or dry-erase markers




Wiring Tracks

  - ❑ A *wiring track* is the space required for a wire
 - 4λ width, 4λ spacing from neighbor = 8λ pitch
- ❑ Transistors also consume one wiring track




Well spacing

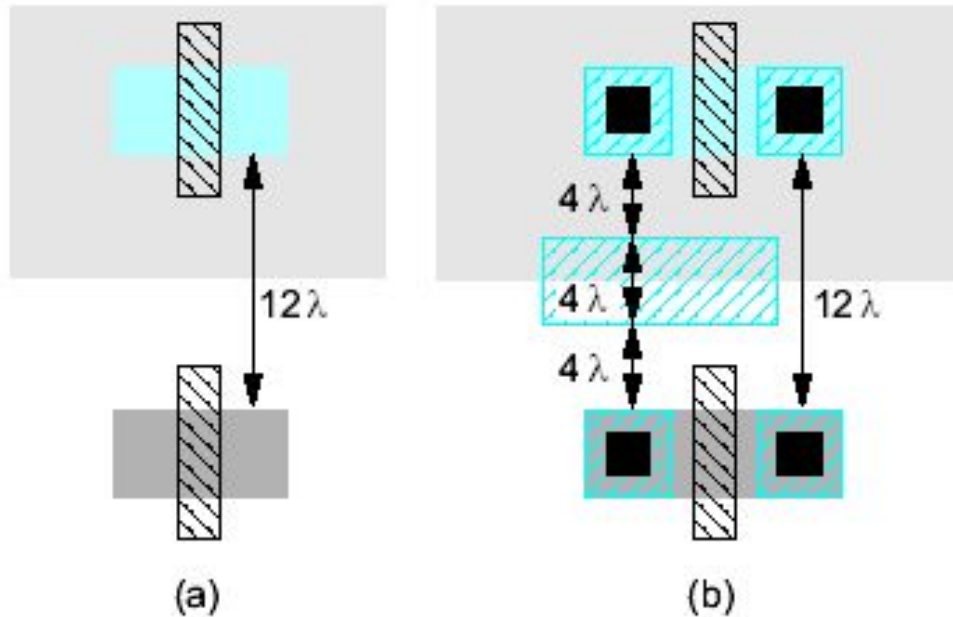- ❑ Wells must surround transistors by 6λ
 - Implies 12λ between opposite transistor flavors
 - Leaves room for one wire track




Area Estimation

 - Estimate area by counting wiring tracks
 - Multiply by 8 to express in λ



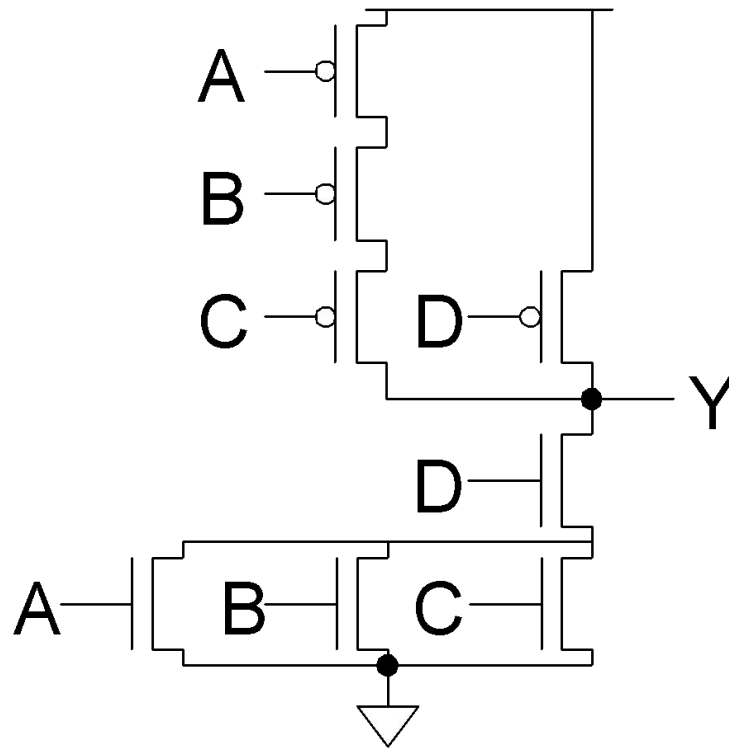Example: O3AI


$$\square \quad Y = \overline{(A + B + C)} \boxtimes D$$



 Example: O3AI

- Sketch a stick diagram for O3AI and estimate area

$$Y = \overline{(A + B + C)} \boxtimes D$$



Example: NOR4

Example: NOR4

