

CSE460: VLSI Design

Lecture 7

CMOS DC Characteristics

Contents

- CMOS Inverter DC Characteristics
- Noise Margin
- nMOS & pMOS Pass Transistor DC Characteristics


Static CMOS Inverter

A static CMOS inverter is built using a pMOS and an nMOS

DC Transfer function or DC response: V_{out} vs V_{in}

For the CMOS inverter shown:


- $V_{in} = 0 \Rightarrow V_{out} = V_{DD}$
- $V_{in} = V_{DD} \Rightarrow V_{out} = 0$
- In between these 2 cases, V_{out} depends transistor current
- V_{out} vs V_{in} relationship can be found by setting $I_{dsn} = |I_{dsp}|$
- V_{out} vs V_{in} relationship can also be found via graphical solutions

 

CMOS Inverter DC Response

CMOS Inverter DC response can be determined as:


1. Divide the input into 5 different regions:
 - a. **A:** $0 \leq V_{in} < V_{tn}$
 - b. **B:** $V_{tn} \leq V_{in} < V_{DD}/2$
 - c. **C:** $V_{in} = V_{DD}/2$
 - d. **D:** $V_{DD}/2 < V_{in} \leq V_{DD} - |V_{tp}|$
 - e. **E:** $V_{in} > V_{DD} - |V_{tp}|$
2. Determine the operating regions of the devices
 - a. Cutoff, Linear or Saturation?
3. Approximate V_{out} at **A**, **B**, **C**, **D** & **E** regions depending on the **pMOS** and **nMOS operating regions**

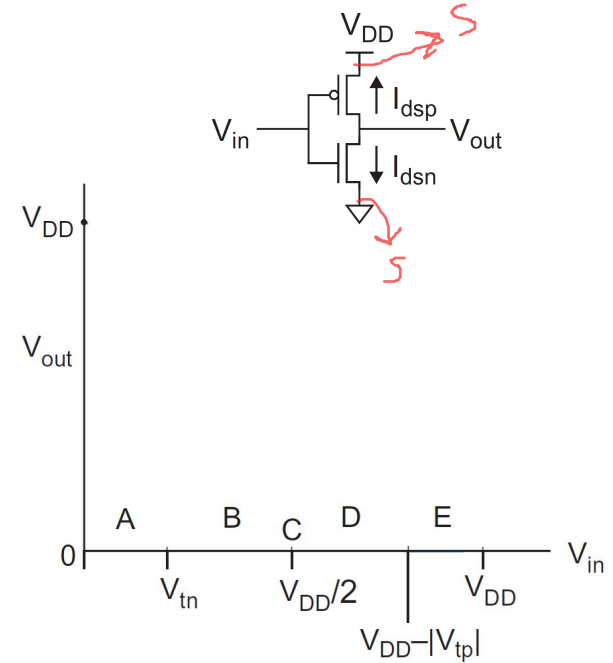

CMOS Inverter DC response

Region A

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

 

$$V_{SD} = 5 - 5 = 0 < |V_{ov}|$$


$$V_{gs} < V_{tn}$$

CMOS Inverter DC response

Region B

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

 As NMOS gets ON now, the V_{out} value is now connected to GND now at same time hence V_{out} degrades from V_{DD} to lower value now




$V_{gs} = V_{in}$; $V_{ds} = V_{out}$

CMOS Inverter DC response

Region C

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	<u>V_{out} drops sharply</u>
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

 NMOS is at its peak performance ie now V_{out} 's previous value ie V_{DD} is now totally degraded due to connection to GND and as saturation occurs for NMOS, I_{Dn} is max now




CMOS Inverter DC response

Region D

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$


as V_{out} has dropped too much, now,
 $V_{sd} = V_{DD} - V_{out} > V_{sg} - |V_t|$

 

CMOS Inverter DC response

Region E

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

 


for PMOS, $V_{sg} = V_{DD} - (V_{DD} - |V_{tp}| + \text{some value}) < |V_{tp}|$

hence, PMOS turns off now

CMOS Inverter DC response

Complete V_{out} vs V_{in}



Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

 

Practical CMOS Inverter DC response

In reality, the sharp change at region C is not that sharp and has finite slope

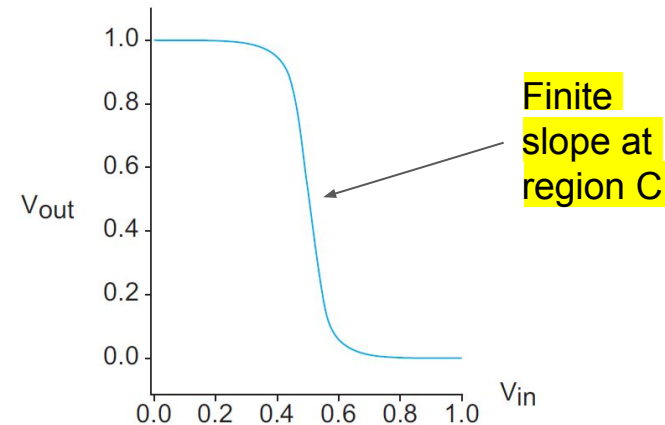 - Theoretical inverter DC response vs Practical inverter DC response






Supply Current

If $I_{DD} = I_{dsn} = |I_{dsp}|$ is the supply current drawn from V_{DD}

- I_{DD} is non-zero in regions B, C & D
- I_{DD} is zero in regions A & E

Region	Condition	p-device	n-device
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated
C	$V_{in} = V_{DD}/2$	saturated	saturated
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear

   

Power Consumption


If $I_{DD} = I_{dsn} = |I_{dsp}|$ is the current drawn from supply V_{DD}

- I_{DD} is non-zero in regions B, C & D
- I_{DD} is zero in regions A & E

That is why we always try to work with strong signals

- A strong 0 falls in the region A where $I_{DD} \approx 0$
- A strong 1 falls in the region E where $I_{DD} \approx 0$

 $I_{DD} \approx 0$ or low implies low power consumption!



Power Consumption


If $I_{DD} = I_{dsn} = |I_{dsp}|$ is the current drawn from supply V_{DD}

- I_{DD} is non-zero in regions B, C & D
- I_{DD} is zero in regions A & E

That is also why we try to avoid degraded signals

- A degraded 0 falls in the region B/C where $I_{DD} \neq 0$
- A degraded 1 falls in the region D/C where $I_{DD} \neq 0$

 $I_{DD} \neq 0$ or high implies high power consumption!



Beta Ratio Effects

$$\beta_n = \mu_n C_{ox} \frac{W}{L}$$


The crossover point, where $V_{in} = V_{out}$ is called the **input threshold, V_{inv}**

For $\beta_p = \beta_n$, the inverter threshold voltage, $V_{inv} = V_{DD}/2$

β_p / β_n is called the **beta ratio; $r = \beta_p / \beta_n$**

- $r = 1 \Rightarrow$ inverter is **un-skewed**
- $r > 1 \Rightarrow$ inverter is **HI-skewed** $\rightarrow V_{inv} > \frac{V_{DD}}{2}$
- $r < 1 \Rightarrow$ inverter is **LO-skewed**

 Thus, by changing r we **can shift the response!**




Beta Ratio Effects for a Static CMOS Inverter

We would like to know how V_{inv} changes for a CMOS inverter as we change r

For the CMOS inverter shown:

- $V_{gsp} = V_{in} - V_{DD}$
- $V_{dsp} = V_{out} - V_{DD}$
- $V_{gsn} = V_{in} - 0 = V_{in}$
- $V_{dsn} = V_{out} - 0 = V_{out}$

Assume: $V_{tp} = -V_{tn}$

 


Beta Ratio Effects for a Static CMOS Inverter

For $\beta_p \neq \beta_n$, we can calculate the inverter threshold voltage by setting $V_{in} = V_{inv}$

1. In region C, both pMOS & nMOS are saturated
2. So the nMOS and pMOS currents are:
 - $I_{dsp} = \beta_p (V_{gsp} - V_{tp})^2 / 2 = \beta_p (V_{inv} - V_{DD} - V_{tp})^2 / 2$
 - $I_{dsn} = \beta_n (V_{gsn} - V_{tn})^2 / 2 = \beta_n (V_{inv} - V_{tn})^2 / 2$
3. Set the currents $I_{dsp} = -I_{dsn}$
4. Solve for V_{inv} :

$$V_{inv} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$


not modulus; put
value with sign

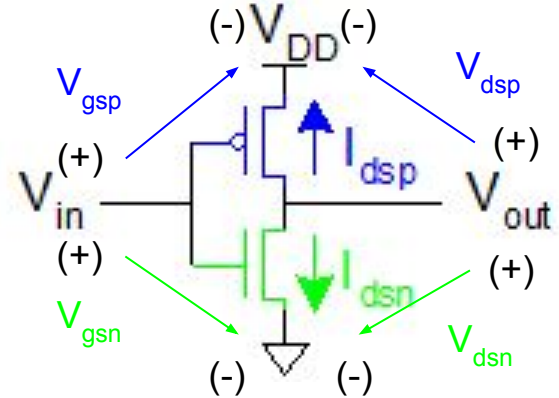

Beta Ratio Effects

So thus for $\beta_p \neq \beta_n$, we can calculate the inverter threshold voltage as a function of “ r ”, where $r = \beta_p / \beta_n$
 
$$V_{\text{inv}} = \frac{V_{DD} + V_{tp} + V_{tn} \sqrt{\frac{1}{r}}}{1 + \sqrt{\frac{1}{r}}}$$



Other CMOS Gates

DC transfer characteristics of other static CMOS gates can be understood by collapsing the gates into an equivalent inverter

- **Series transistors** can be viewed as a single transistor of greater length
- If only one of several **parallel transistors** is ON, the other transistors can be ignored
- If several **parallel transistors** are ON, the collection can be viewed as a single transistor of greater width

Noise Margin (Noise Immunity)

Noise margin is closely related to the DC voltage characteristics

Helps determine the allowable noise voltage on the input of a gate so that the output will not be corrupted

The specification most commonly used to describe noise margin uses two parameters:

1. The LOW noise margin, NM_L
2. The HIGH noise margin, NM_H

Noise Margin

Voltage definitions:

V_{IH} = minimum HIGH input voltage

V_{IL} = maximum LOW input voltage


V_{OH} = minimum HIGH output voltage

V_{OL} = maximum LOW output voltage

NM_L = The LOW noise margin

NM_H = The HIGH noise margin

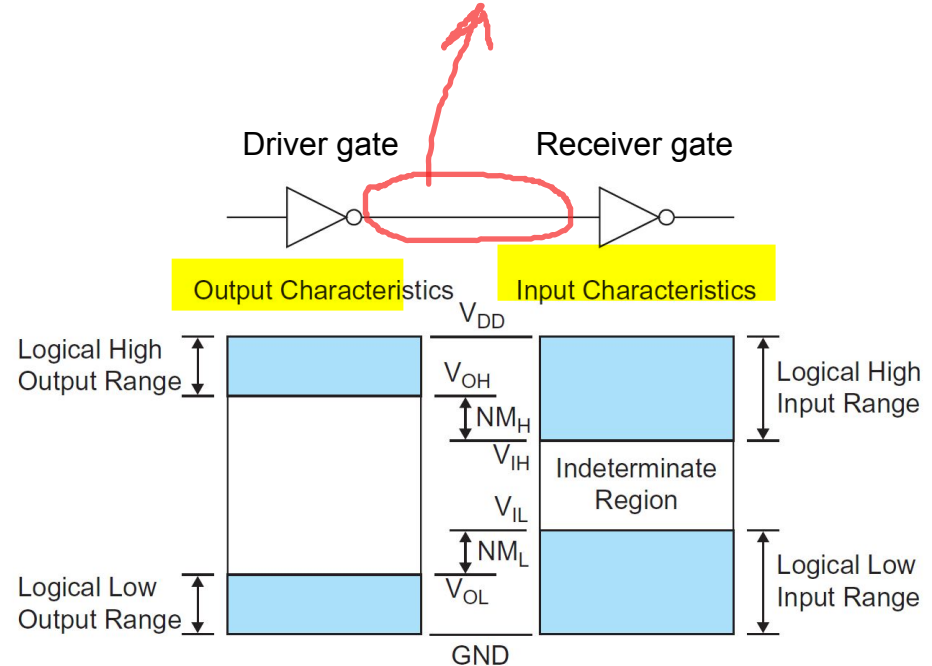
noise prone hence receiver may receive voltage between V_{OH} and V_{OL} range so we need noise margin now



Low Noise Margin

- The **LOW noise margin (NM_L)** is the difference in maximum LOW input voltage recognized by the receiving gate and the maximum LOW output voltage produced by the driving gate


$$NM_L = V_{IL} - V_{OL}$$

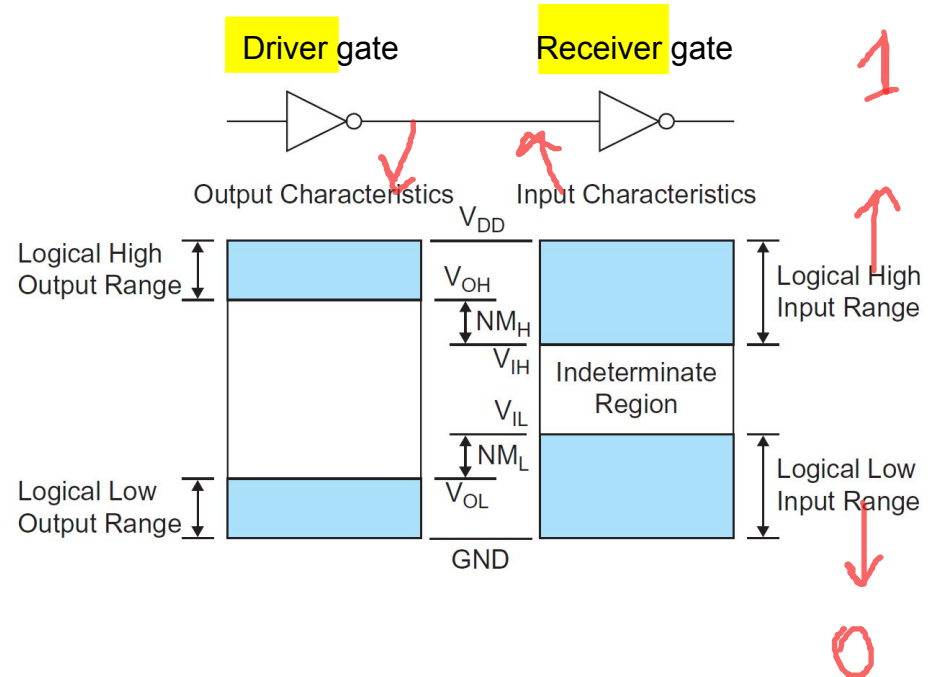

High Noise Margin

- The **HIGH** noise margin (NM_H) is the difference between the minimum HIGH output voltage of the driving gate and the minimum HIGH input voltage recognized by the receiving gate


$$NM_H = V_{OH} - V_{IH}$$

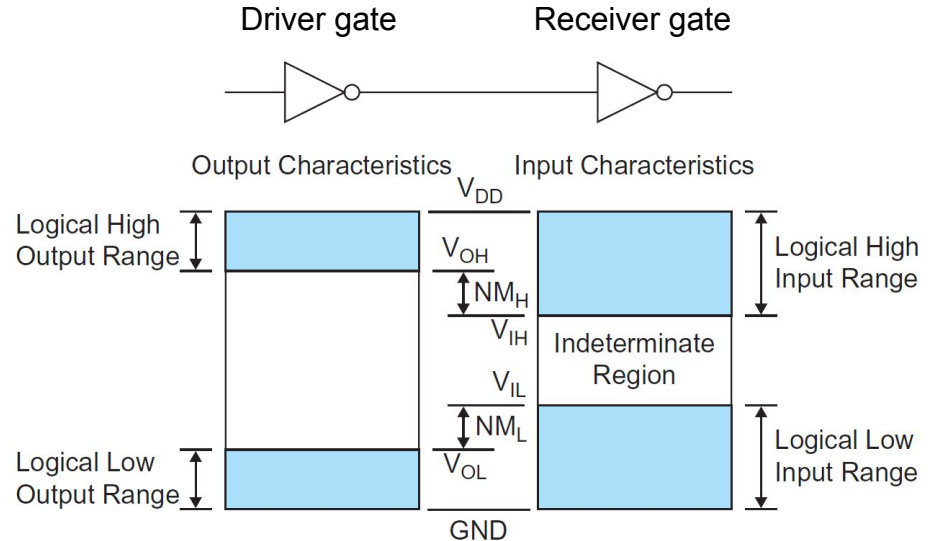

Selecting V_{IL} , V_{IH} , V_{OL} & V_{OH}

How to choose the logic levels V_{IL} , V_{IH} , V_{OL} & V_{OH} such that the noise margins NM_L & NM_H are maximized?


- Use the DC transfer characteristics!

 

Selecting V_{IL} , V_{IH} , V_{OL} & V_{OH}

How to choose the logic levels V_{IL} , V_{IH} , V_{OL} & V_{OH} such that the noise margins NM_L & NM_H are maximized?

 
- Use the DC transfer characteristics!
- Logic levels are defined at the unity gain point where the slope is -1
- This gives a conservative bound on the worst case static noise margin



Selecting V_{IL} , V_{IH} , V_{OL} & V_{OH}


Logic levels of typical 5 V and 3.3 V logic families

Logic Family	V_{DD}	V_{IL}	V_{IH}	V_{OL}	V_{OH}
TTL	5 (4.75–5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5–6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3–3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3–3.6)	0.9	1.8	0.36	2.7

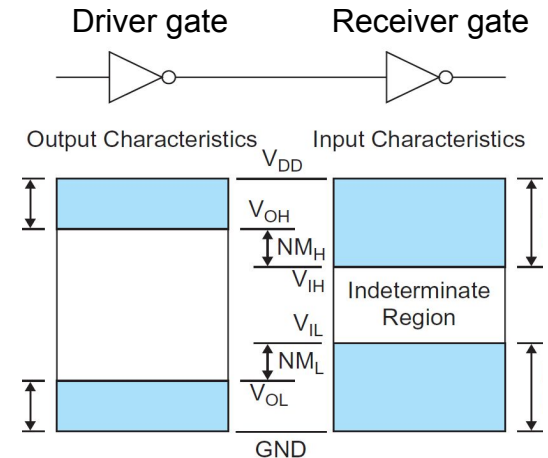

Noise Margin: Summary

 
- **NM_L or NM_H too small:** the gate may be disturbed by noise that occurs on the inputs
- An **unskewed gate** has equal noise margins: which maximizes immunity to arbitrary noise sources
- If a gate sees more noise in the high or low input state: the gate can be skewed to improve that noise margin at the expense of the other



Noise Margin: Summary

- **Noise sources tend to scale with the supply voltage:** so noise margins are best given as a fraction of the supply voltage; for example $0.3V_{DD}$

 A noise margin of 0.4 V is quite comfortable in a 1.8 V process, but marginal in a 5 V process



Pass Transistor DC Characteristics

Recall from our previous lectures that


- **nMOS** transistors pass '0's well but '1's poorly
- **pMOS** transistors pass '1's well but '0's poorly

We are now better prepared to define how “poorly”

nMOS Pass Transistor DC Characteristics

To keep an nMOS transistor ON, we need

 
- $V_{gs} \geq V_{tn}$
- $\Rightarrow V_g - V_s \geq V_{tn}$
- $\Rightarrow V_s \leq V_g - V_{tn}$
- $\Rightarrow V_{s(max)} = V_g - V_{tn}$



nMOS Pass Transistor DC Characteristics

To keep an nMOS transistor ON, we need

- $V_{s(\max)} = V_g - V_{tn}$

 

nMOS transistors passing '1' ($V_{in} = V_{DD}$; $V_{out} = ?$)


- Gate is connected to V_{DD} : $V_g = V_{DD}$
- Current flowing from drain to source
- $V_{in} = V_d = V_{DD}$; $V_{out} = V_s = ?$
- But we know $V_{s(\max)} = V_g - V_{tn} \Rightarrow V_{out(\max)} = V_{DD} - V_{tn}$

nMOS transistors attempting to pass a '1' **never pass above $V_{DD} - V_{tn}$**

pMOS Pass Transistor DC Characteristics

To keep a pMOS transistor ON, we need

- $V_{sg} \geq |V_{tp}|$
- $\Rightarrow V_s - V_g \geq |V_{tp}|$
- $\Rightarrow V_s \geq V_g + |V_{tp}|$
- $\Rightarrow \mathbf{V_{s(min)} = V_g + |V_{tp}|}$

 

pMOS Pass Transistor DC Characteristics


To keep a pMOS transistor ON, we need

- $V_{s(\min)} = V_g + |V_{tp}|$

pMOS transistors passing '0' ($V_{in} = 0$; $V_{out} = ?$)

- Gate is connected to GND: $V_g = 0$
- Current flowing from source to drain
- $V_{in} = V_d = 0$; $V_{out} = V_s = ?$
- But we know $V_{s(\min)} = V_g + |V_{tp}| \Rightarrow V_{out(\min)} = |V_{tp}|$

pMOS transistors attempting to pass a '0' never pass lower than $|V_{tp}|$

 

but if this vol=VDD: Now, it's the source end as Source of PMOS is always at higher voltage than drain


hence now, V_{out} ie V_{drain} fully charges to VDD

nMOS Pass Transistor DC Characteristics

Series nMOS transistors passing '1' (V_{DD})

- If all of the transistors have gates tied to V_{DD}
- $V_{g(T1)} = V_{g(T2)} = V_{g(T3)} = V_{DD}$
- $V_{in(T1)} = V_{DD}$; $V_{out(T3)} = ?$

drain

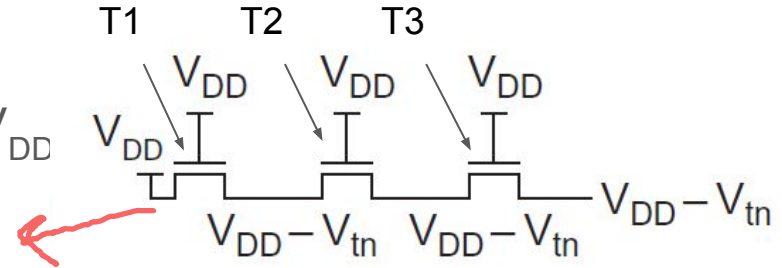

1. Output of Transistor T1: $V_{out(max), T1} = V_{g(T1)} - V_{tn(T1)} = V_{DD} - V_{tn}$
2. Output of Transistor T2: $V_{out(max), T2} = V_{g(T2)} - V_{tn(T2)} = V_{DD} - V_{tn}$
3. Output of Transistor T3: $V_{out(max), T3} = V_{g(T3)} - V_{tn(T3)} = V_{DD} - V_{tn}$

nMOS Pass Transistor DC Characteristics


nMOS transistor driven by degraded output

- If T1 transistor has gate tied to V_{DD}
- $V_{g(T1)} = V_{DD}$; $V_{in} = V_{DD}$; $V_{out} = ?$

Output of Transistor T1: $V_{out(max), T1} = V_{g(T1)} - V_{tn(T1)} = V_{DD} - V_{tn}$

- Output of transistor T1 is now driving the gate of transistor T2
- T2 transistor has gate tied to $V_{DD} - V_{tn}$
- $V_{g(T2)} = V_{DD} - V_{tn}$; $V_{in} = V_{DD}$; $V_{out} = ?$

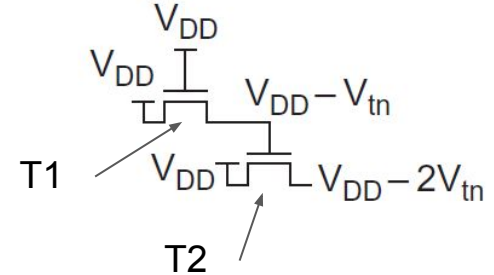
Output of Transistor T2: $V_{out(max), T2} = V_{g(T2)} - V_{tn(T2)} = (V_{DD} - V_{tn}) - V_{tn} = V_{DD} - 2V_{tn}$



Pass Transistor DC Characteristics: Summary


nMOS pass transistor

 - $V_{in} = \text{GND} \Rightarrow V_{out} = \text{GND}$ (strong 0)
- $V_{in} = V_{DD} \Rightarrow V_{out(max)} = V_g - V_{tn}$ (degraded 1)



pMOS pass transistor

- $V_{in} = \text{GND} \Rightarrow V_{out(min)} = |V_{tp}|$ (degraded 0)
- $V_{in} = V_{DD} \Rightarrow V_{out} = V_{DD}$ (strong 1)

 

Pass Transistor DC Characteristics: Summary

- nMOS/pMOS pass transistors sometimes produce degraded outputs
- The loss is sometimes called a threshold drop
- In old processes where V_{DD} was high and V_t was a small fraction of V_{DD} , the threshold drop was tolerable
- In modern processes V_{DD} is significantly lower and V_t is almost $\frac{1}{3}$ of V_{DD} , the threshold drop can produce an invalid or marginal logic at the output

To solve this problem we use CMOS transmission gates