
 
 
 
 
 
 
 
 


Signal Strength

- ❑ *Strength* of signal
 - How close it approximates ideal voltage source
- ❑ V_{DD} and GND rails are strongest 1 and 0
- ❑ nMOS pass strong 0
 - But degraded or weak 1
- ❑ pMOS pass strong 1
 - But degraded or weak 0
- ❑ **Thus nMOS are best for pull-down network**
- ❑ **And, pMOS are best for pull-up network**


Pass Transistors

- Transistors can be used as switches

 

Pass transistor

N-MOS pass transistor:

 

For NMOS → Source is at lower potential
Drain is at higher "

reason = ??
↓

Source to Drain
 e^- is sent by
repulsion at Source and
hence Source is at (-ve)
potential.

Case 1: $A=1, B=0$:

here, B = lower potential than Y hence its ~~the~~ Source now.

C_L discharges through MOS to GND at B point.

for NMOS, $V_{gs} > V_{th}$ to be ON. Hence C_L ie Y

Node can be fully discharged in this case → Good 0.
→ always $V_{gs} = 5 - 0 = 5V > V_{th}$

not exactly AND
due to Z

A	B	$Y = A \cdot B$
0	0	0
0	1	0
1	0	0 → good '0'
1	1	1 → Bad '1'

Case 2: $A=1, B=1$:

Now, B is at (+5V) ie highest potential hence its
now the drain end. Y is the source now.

C_L starts getting charged from $B \rightarrow NMOS \rightarrow Y$ node.

But as $V_{gs} > V_{th}$ [let, $V_{th} = 1V$ here]


$$\Rightarrow V_g - V_s > 1 \Rightarrow V_s < (5 - 1)$$

$$\Rightarrow V_s < 4V$$

Hence, the source ie Y node can rise upto 4V only
in ON state so, 4V instead of 5V

↓
Bad 1

PMOS Pass transistor

 

A	B	$Y = \bar{A} \cdot B$
0	0	0 → bnd
0	1	1 → good
1	0	0
1	1	0

not exactly
AND
due to
2 state

PMOS ON condition: $V_{sg} > |V_{tp}|$

Also, for PMOS → source is at Higher potential
to repel holes from S → D end

→ Drain is at lower potential

Case 1: A = 0, B = 0:

here, B = Drain end hence if C_L is already charged beforehand
it starts discharging to GND at B node. As for PMOS →

$$V_{sg} > |V_{tp}| \quad [k_t, |V_{tp}| = 1V]$$

$$\Rightarrow V_s > (1 - 0) V$$

Hence, the Y node is source node will stop discharging
when its slightly higher than 1V.

↓

Bad 0 hence

Case 2: A = 0, B = 1:

Now, B = High potential = hence its Source now.

As A = 0, the Y node ie C_L starts getting charged
due to (+5V) at B node.

Y node = Drain now



$V_{sg} > |V_{tp}|$ → always maintained no matter whatever
voltage appears at Y node. C_L always now $V_{sg} = (5 - 0)$
= 5V > |V_{tp}|

↓

Hence Y node capacitance can fully get charged
to +5V so good 1 ensured

4 to 1 Mux using NMOS Pass T

  
$$Y = \bar{S}_0 \bar{S}_1 D_0 + S_0 \bar{S}_1 D_1 + \bar{S}_0 S_1 D_2 + S_0 S_1 D_3$$




- NMOS needed = 8
- Also, passes 1 poorly as seen earlier [V_{th} drop]

Transmission Gates

 
- ❑ Pass transistors produce **degraded** outputs
- ❑ *Transmission gates* pass both 0 and 1 well



Transmission Gate (TG)

 

internal components $\rightarrow$

 

Case 1: $S=1, A=0$:

Both MOS are ON. For NMOS $\rightarrow A = \text{source}, Y = \text{drain}$
 For PMOS $\rightarrow A = \text{drain}, Y = \text{source}$

$A=0$ hence good 0 will pass through the NMOS now
 without any drop loss. $Y = \text{totally discharged to '0'}$

Case 2: $S=1, A=1$:

Both MOS = ON $\rightarrow$ For NMOS $\Rightarrow A = \text{drain}, Y = \text{source}$
 For PMOS $\Rightarrow A = \text{source}, Y = \text{drain}$


to pass 1 from A to Y, PMOS will participate
 and charges C_L to (+5V) exactly.

S	A	Y
0	0	$\bar{z}$
0	1	$\bar{z}$
1	0	good 0
1	1	good 1

$\rightarrow$ coz A and Y nodes are
 totally disconnected.

SOP $\Rightarrow Y = S \cdot A \rightarrow$ not exactly AND operation
 due to $\bar{z}$ state



4 to 1 mux using TG

 

Tristates


- ❑ *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  


Nonrestoring Tristate

 - ❑ Transmission gate acts as tristate buffer
 - Only two transistors
 - But *nonrestoring*
 - Noise on A is passed on to Y



Tristate Inverter

 
- ❑ Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Multiplexers


- ❑ 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 


Gate-Level Mux Design

 - ❑ $Y = SD_1 + \bar{S}D_0$ (too many transistors)
- ❑ How many transistors are needed? = **20** (2 for S_bar, 6*2 for AND, finally 6 for OR)




these are transistor count


 


Transmission Gate Mux

 - ❑ Nonrestoring mux uses two transmission gates
 - Only 4 transistors << 20 in prev slide





Logic Gate using TG

  

AND

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1



Logic Gate using TG

  

OR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1


Logic Gate using TG

  


XOR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0

2:1 MUX using TG

 

Block Diagram:

 




INPUTS	Output
S_0	Y
0	A_0
1	A_1

The logical expression of the term Y is as follows:

$$Y = S_0' \cdot A_0 + S_0 \cdot A_1$$

Inverting Mux

   - ❑ Inverting multiplexer
 - Use compound AOI22
 - Or pair of tristate inverters
 - Essentially the same thing
- ❑ Noninverting multiplexer adds an inverter





4:1 Multiplexer

S_1	S_0	f
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

$$\rightarrow f = \overline{S_1} \overline{S_0} D_0 + \overline{S_0} \overline{S_1} D_1 + S_1 \overline{S_0} D_2 + S_0 S_1 D_3$$

  
4:1 Multiplexer

- ❑ 4:1 mux chooses one of 4 inputs using two selects
 - Two levels of 2:1 muxes
 - Or four tristates



Logic Gates using Multiplexer

And Gate Using 2:1 MUX

 

$B \rightarrow I_1$
 $A \rightarrow S$
 $I_0 \rightarrow 0V$



AND

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1



Logic Gates using Multiplexer

NAND Gate using MUX

A	B	OUT
0	0	1
0	1	1
1	0	1
1	1	0


OUT = 1
when A = 0

OUT = B'
when A = 1

  


Logic Gates using Multiplexer

OR Gate Using 2:1 MUX

 

 $B \rightarrow I_0$
 $A \rightarrow S$
 $I_1 \rightarrow 5V$



OR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1


Logic Gates using Multiplexer

NOR Gate using MUX

A	B	OUT
0	0	1
0	1	0
1	0	0
1	1	0

OUT = B' when A = 0


OUT = 0 when A = 1

 

NAND-3 gate implementation using one mux only


Way 1: using a 4:1 mux:

hint: take MBs as select pins

 


A	B	C	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

Way 2: using one 8:1 mux:

 

using two 2:1 muxs only:

 

Difference between combinational and sequential circuits



Combinational Circuit	Sequential Circuit
This output is solely dependent on the current input.	This output is affected by both current and previous input.
The process is quick.	The process is slow.
It is intended to be simple.	When compared to combinational circuits, it is more efficiently designed.
There is no feedback from input to output.	A feedback path exists between input and output.
This is not dependent on time.	This is time-sensitive.
Basic building blocks: Logical gates	Basic building blocks: Flip-flops
Used for both arithmetic and boolean operations.	Mostly used for data storage.
Combinational circuits are incapable of storing any state.	Sequential circuits can store any state or retain previous states.
Combinational circuits do not require triggering because they lack a clock.	Sequential circuits require triggering because they are clock dependent.
These circuits lack a memory element.	Memory elements are used in these circuits.
It is simple to use and manage.	It is difficult to use and handle.

Combinational circuits are built with logic gates such as AND, OR, NOT, NAND, and NOR. These logic gates serve as the foundation for combinational circuits.

Sequential circuits are built with counters, shift registers, latches, etc.


D Latch

  - ❑ When $CLK = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- ❑ When $CLK = 0$, the latch is *opaque*
 - Q holds its old value independent of D
- ❑ a.k.a. *transparent latch* or *level-sensitive latch*




D Latch Design using MUX

- ❑ Multiplexer chooses D or old Q



 


+ve D Latch Design using Transmission gate

It's a Positive level triggered D-Latch

 


+ve D Latch Operation

   

-ve D Latch Design using Transmission gate


It's a Negative level triggered D-Latch.

Replaced CLK with CLK_bar.

 


D Flip-flop

 - ❑ When CLK rises, D is copied to Q
- ❑ At all other times, Q holds its value
- ❑ a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*




+ve edge triggered D Flip-flop Design by cascading -ve Latch with +ve Latch in series

 - ❑ Built from master and slave D latches






D Flip-flop Operation

 

When CLK=0: Q retains it's old value and QM_bar = D_bar is being continuously set unless CLK=1

When CLK=1: D gets disconnected from QM_bar line hence QM_bar=D_bar is sent directly to Inverter to Q point.

   
Also, after CLK=1 is set, Q can't follow D anymore as D is isolated from QM_bar



-ve edge triggered D Flip-flop Design


by cascading +ve Latch with -ve Latch in series

- ❑ Built from master and slave D latches

 

Design 6:1 mux using 4:1 mux

	S_2	S_1	S_0	f
{	0	0	0	w_0
	0	0	1	w_1
	0	1	0	w_2
{	0	1	1	w_3
	1	0	0	w_4
	1	0	1	w_5

 

keep 10,11 disconnected

→ 01, 11 will never be selected due to GND connection at LSB select pin

Implement boolean expression using Pass Transistor and Transmission gate


$$f = x_2 + x_1 x_3 \rightarrow \text{implement using pass T and TG}$$

x_1	x_3	f
0	0	0
0	1	0
1	0	0
1	1	1

$\left. \begin{matrix} 0 & 0 & 0 \\ 0 & 1 & 0 \\ 1 & 0 & 0 \end{matrix} \right\} \text{always GND}$
 $\left. \begin{matrix} 1 & 1 & 1 \end{matrix} \right\} x_3 \text{ to copy}$


x_2	f'	f
0	0	0
0	1	0
1	0	1
1	1	1

 $\left. \begin{matrix} 0 & 0 & 0 \\ 0 & 1 & 0 \end{matrix} \right\} f' \text{ to copy}$
 $\left. \begin{matrix} 1 & 0 & 1 \\ 1 & 1 & 1 \end{matrix} \right\} \text{always +5V}$




→ using NMOS pass transistors

using TG:

 


Pass Transistor math

[5 marks] In the **adjacent figure**, the supply voltage (V_{DD}) is 5 V. The threshold voltages for the pMOS and nMOS transistors are both set at $V_{tn} = |V_{tp}| = 0.1$ V. **Determine** the voltages V_1 , V_2 , V_3 , and V_4 as well as the output voltages V_X and V_Y . [**Z is also a valid output.**]

 

Summer 24 → set 2

4(e)

 

$V_{th} = |V_{tp}| = 0.1V$; $V_{DD} = 5V$ (given)

① → ON ; $V_1 = (V_{s,max} \text{ जति} = (V_g - V_{th})) = V_{D1} \text{ वर pass}$
 $= 5 - 0.1 = (4.9V)$

② → ON as $V_g - V_{th} = 4.9 - 0.1 > 0V$

now, V_{S2} ie $V_{1,max} = V_{g2} - V_{th} = 4.9 - 0.1$
 $= (4.8V)$

hence, $V_{D2} = 5V \rightarrow$ gets degraded as $V_{L\text{ mode}}$

$$V_2 = (4.8V)$$

(3) $\rightarrow V_{g3} = 4.8V > 0.1V$ hence ON.

$$V_{3, \max} \text{ (eq. 2)} = V_{g3} - V_{th} = (4.7V)$$

$$V_{p3} = 5V \text{ here} \rightarrow V_3 = V_{s3} = 4.7V$$

(4) $\rightarrow$ pmos of T4 is disabled only nmos is

$$\text{ON. } V_{g4} = 5V \text{ here and, } V_{4, \max} = V_{DD} - 0.1 = (4.9)V$$

$$\text{as } V_{D4} = V_3 = 4.7V < 4.9V \rightarrow V_3 \text{ easily}$$

passes without degradation



$$V_4 = 4.7V$$

(5) $\rightarrow$ PMOS always ON and for PMOS $\rightarrow$

$$V_{sg} > |V_{tp}|$$

$$\Rightarrow V_{s, \min} = V_g + |V_{tp}| \rightarrow V_{ss, \min} \text{ for}$$

$$\therefore V_{ss} = V_4 = \text{given } 1 = 4.7V$$

(6) $\rightarrow V_{g6}$ of NMOS = $4.7V > 0.1V$ hence


ON. $V_{D6} = 5V$ but ~~$V_{D6} = 5V$~~

$V_{S6, \max}$ i.e. $V_{x, \max} = 4.7 - 0.1 = 4.6V$ possible

hence $V_{S6} = V_x = 4.6V$

(7) $\rightarrow$ NMOS always off as $V_g = 0 < V_{th}$

hence, $V_y = \text{floating} = Z$

 

42

Transmission gates are used to execute different types of combinational and sequential logic circuits like below:


 


Figure 1: Circuit on the left is represented by the block **Device 1**. Circuit on the right uses this **Device 1**.

 

(b) **Identify** Device 1 in **Fig. 1** (Negative-edge/level-triggered or positive-edge/level-triggered flip-flop/latch) with a proper **characteristic table. 2**

(c) **Draw** the waveforms in the grid given above for the right circuit of Fig. 1. **Determine** if the circuit is a negative-edge/level-triggered or positive-edge/level-triggered flip-flop/latch?

(b) Device - 1 is a positive level triggered latch.

clk	Q_{n-1}	Q_n
0	0	0/1
0	1	0/1
1	0	0
1	1	1

clk	D	Q_{n-1}	Q
0	0	0	0
0	1	1	1
1	0	0	0
1	1	1	1

(c) positive-edge triggered flip-flop.

